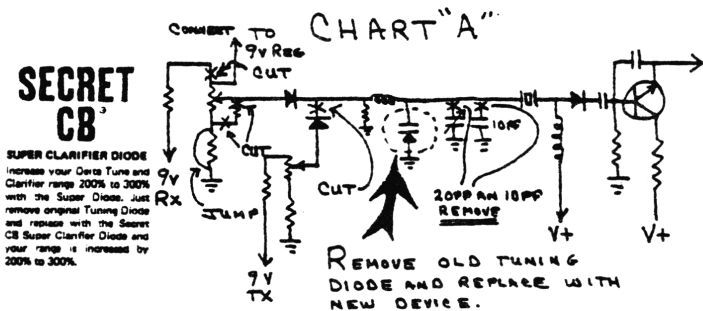


SLIDE INCREASE APPLICATION ON ALL SIDEBAND RADIOS

8KHZ - 12KHZ - 20KHZ+


PARTS NEEDED:

1. Super Clarifier Diode
2. Super Slider



858 UNIDEN CHASSIS WILL USE 3 DIODES LOCATED NEARBYTALS.
 IN MOST APPLICATIONS PRODUCES 8KHZ DOWN

CHART "B"


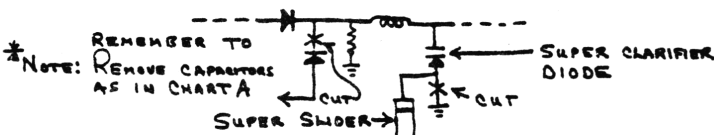


IN MOST APPLICATIONS COMBINATION PRODUCES 20KHZ+

CHART "C"




IN MOST APPLICATIONS PRODUCES 12 KHZ

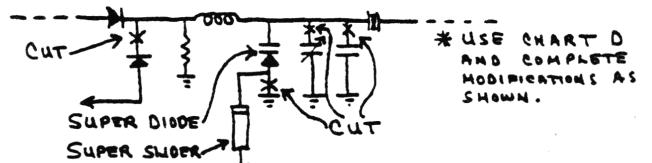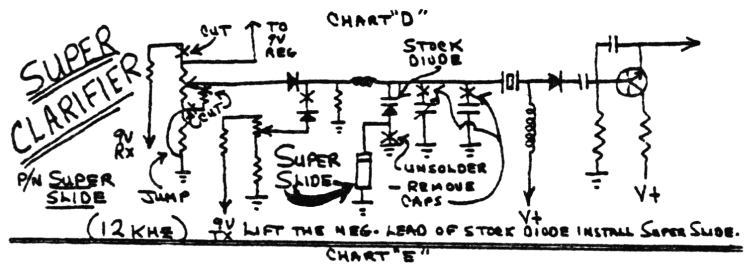

20KHZ APPLICATION*

(OPTIONAL) CHART "F"

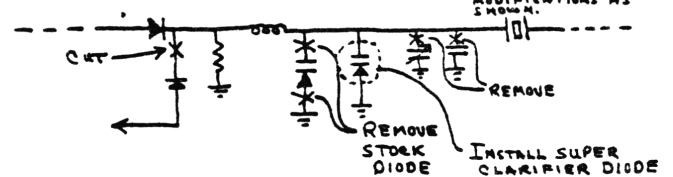

8 KHZ APPLICATION

HELPFUL HINTS

Most UNIDEN chassis will use "THREE DIODES" OR THREE "SUPER SLIDES" OR A COMBINATION OF BOTH. FOR USING THE SUPER CLARIFIER DIODE USE CHARTS A, B, AND C. ALSO F. FOR USING THE SUPER CLARIFIER USE CHARTS D AND E. DO NOT BE ALARMED IF THE SUPER CLARIFIER READS SHORT ON YOUR METER. OBSERVE POLARITY AND INSTALL PER DIRECTIONS.