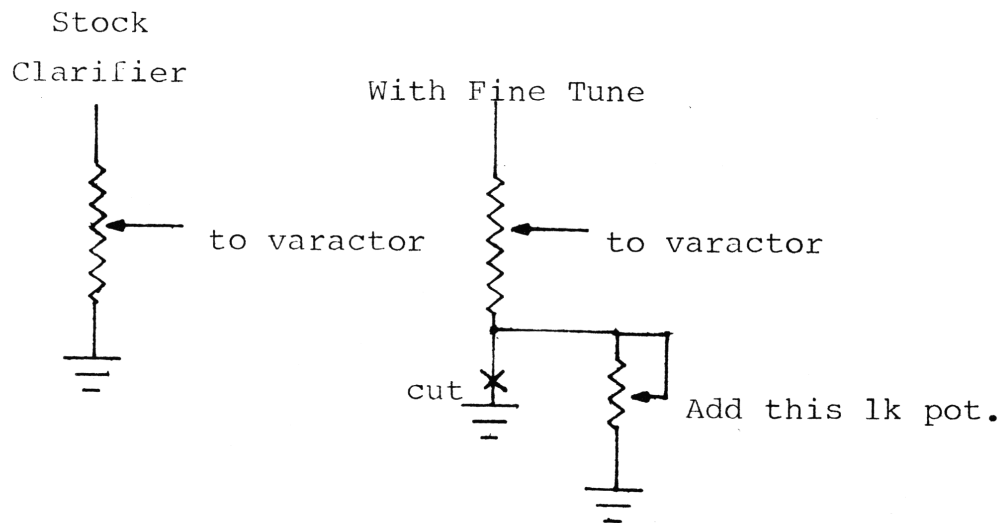


ADD A FINE TUNE TO YOUR CLARIFIER LIKE 2000 GTL



1. Unsolder Clarifier from ground. (sometimes there will be a resistor in series-if so, remove resistor)
2. Drill a hole in any convenient place and mount the additional 1K control.
3. Run a jumper wire from the stock pot over to the new one. One end and wiper should be connected together as shown above. Ground the remaining end of the 1K pot.

If you wish, the stock pot could be replaced with a dual pot as in the 2000 GTL.

The above circuit really works. NEAT! Now you can have 10-20KC Slide on your "Course" Control and about .5KC on your "Fine" control.