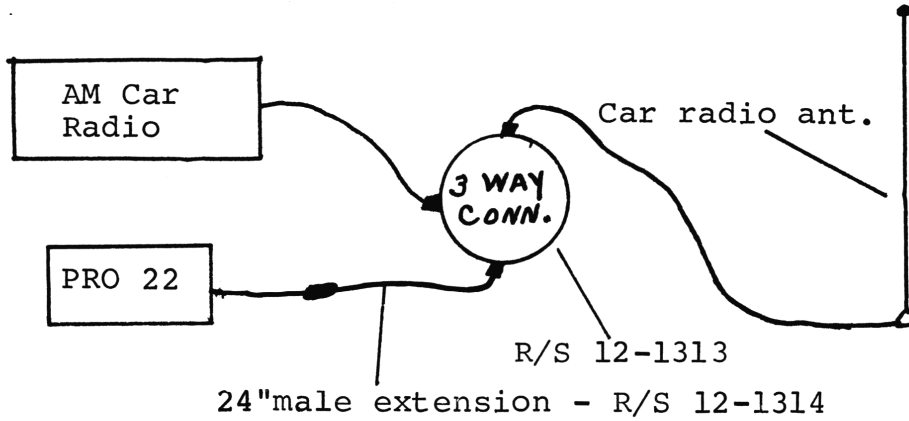


PRO-22 Pocket Scan AM/FM continued:




SET WORKS WITHIN 15 MILES OF DOWNTOWN!

"OOPS, WE GOOFED"



VOL. 12, Page 7: MOTOROLA CM555 - Clarifier, Step 1, should read: Cut off the wire on the end of the clarifier pot which reads 8V on RX, 0V TX. Tape it. Run a new wire from the pot where the original wire was to pin 1 of IC702 (+side of C734).

VOL. 13, Page 63: ROBYN T240D -

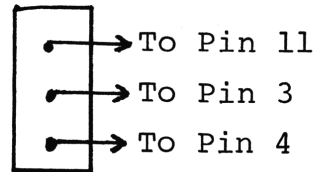

VOL. 14, Page 12: CRAIG L321 - CORRECTED DRAWING - DO NOT CUT the traces as shown before and resistors in new location.

