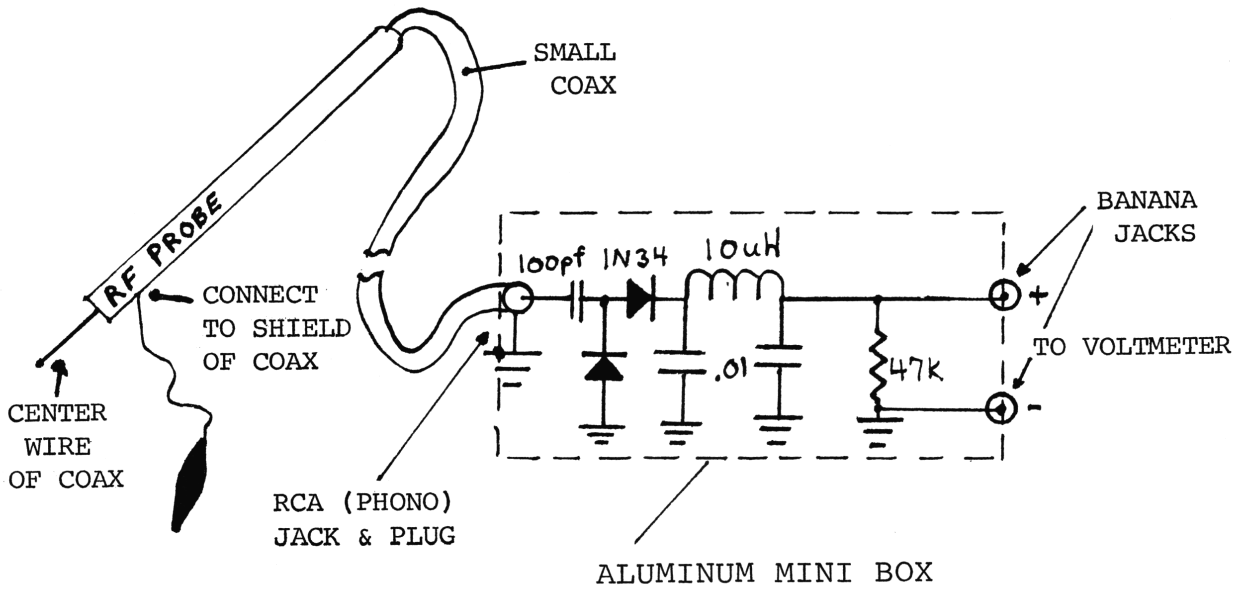



OSCILLATOR CHECKER

THIS RF PROBE IS HANDY FOR OSCILLATOR CHECKS:



LOW CAPACITY PROBE

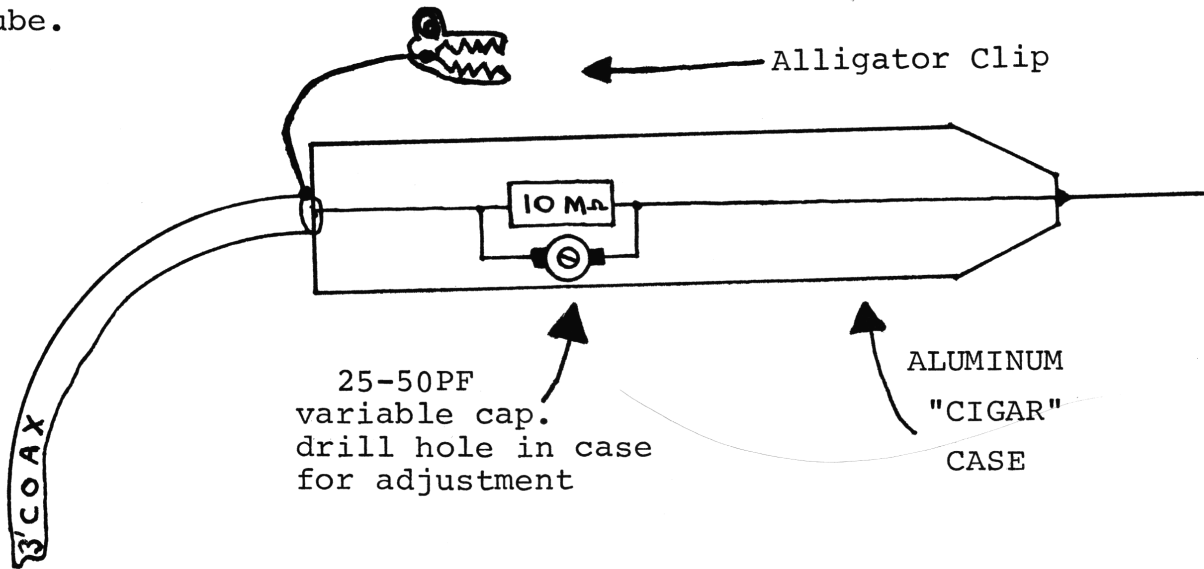A necessity for RF work, prevents loading. Put in a shielded tube.



Feed in square wave signal and adjust trimmer cap for best waveform:

