70 WATT BASE LINEAR
MAIN SCHEMATIC

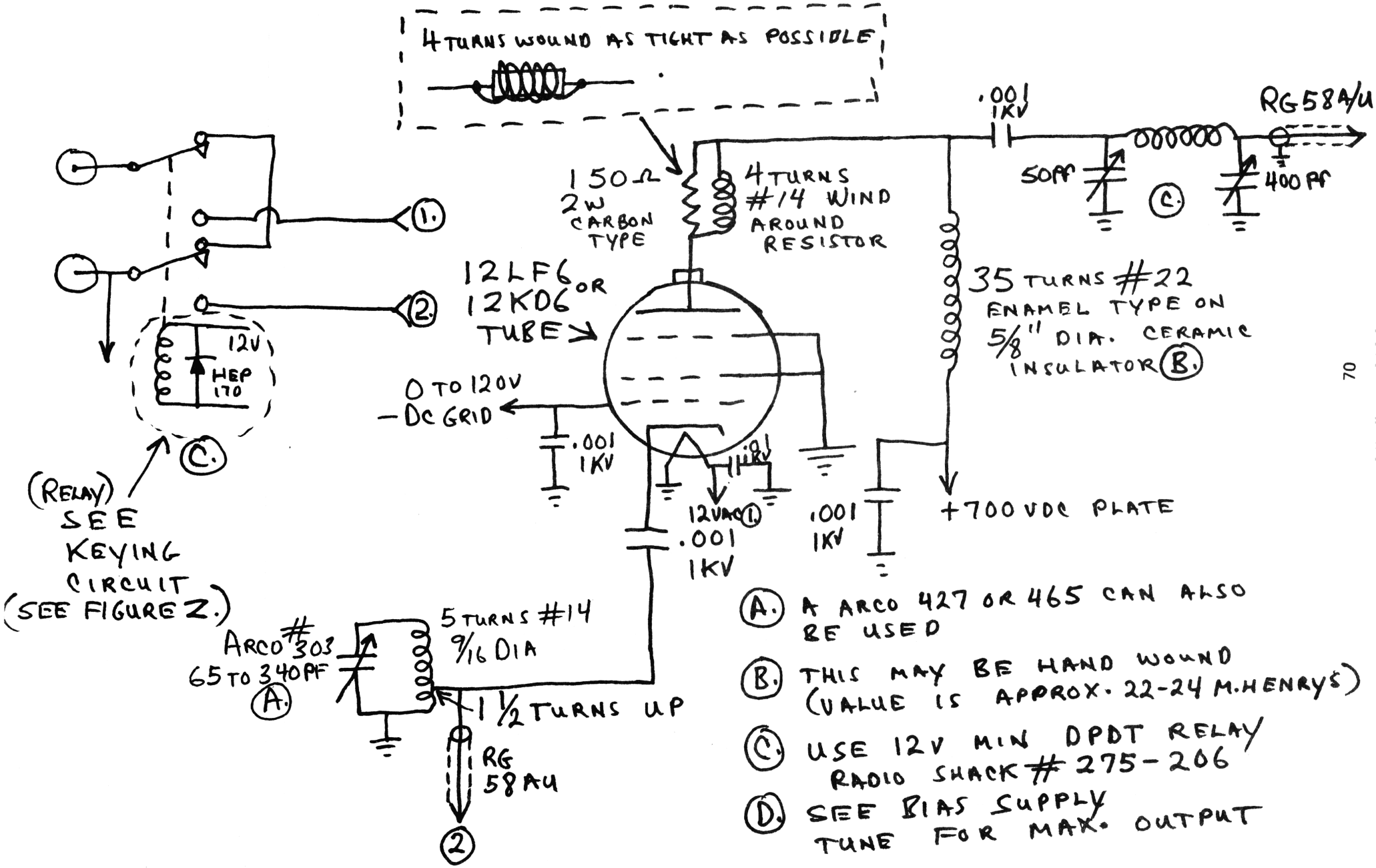

(A.) A ARCO 427 OR 465 CAN ALSO BE USED

(B.) THIS MAY BE HAND WOUND (VALUE IS APPROX. 22-24 M.HENRYS)

(C.) USE 12V MIN DPDT RELAY RADIO SHACK # 275-206

(D.) SEE BIAS SUPPLY TUNE FOR MAX. OUTPUT

70

http://www.cbtricks.com

70 WATT
BASE LINEAR (SEE MAIN SCHEMATIC)
KEYING CIRCUIT AND/ POWER SUPPLY DIAGRAMS

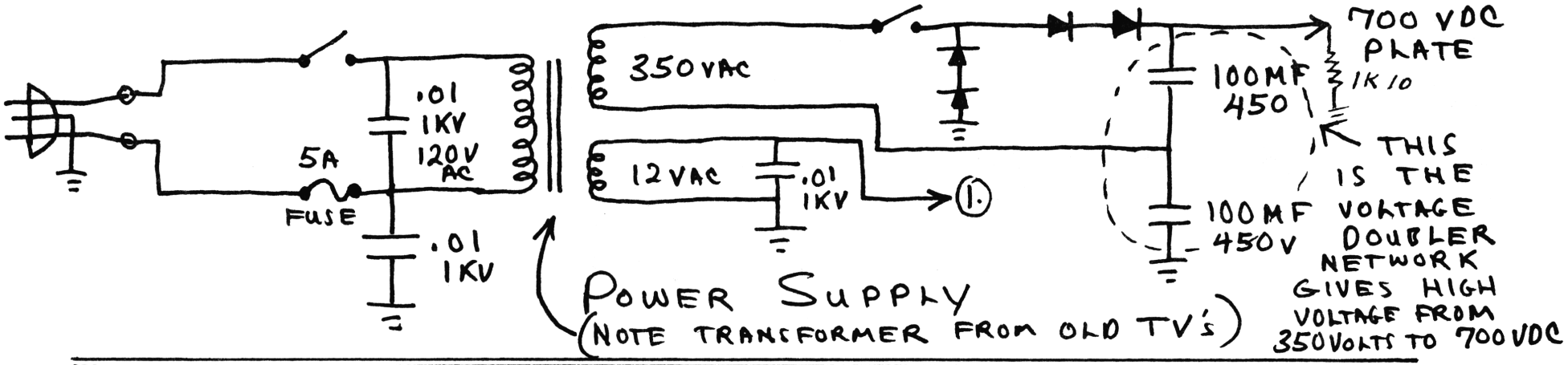

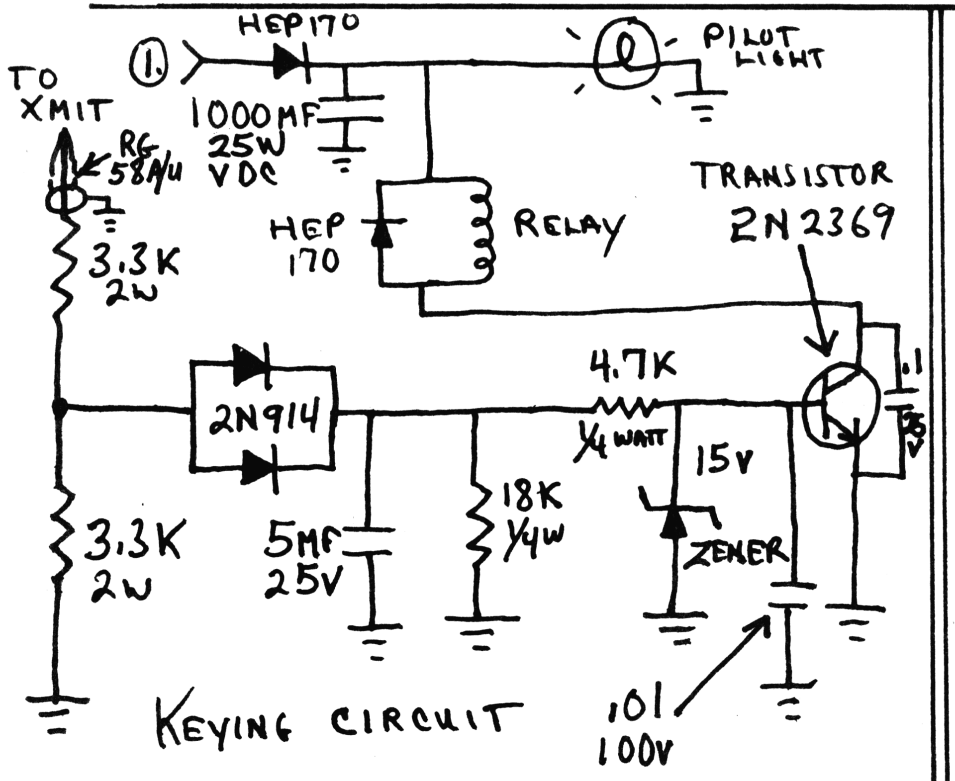

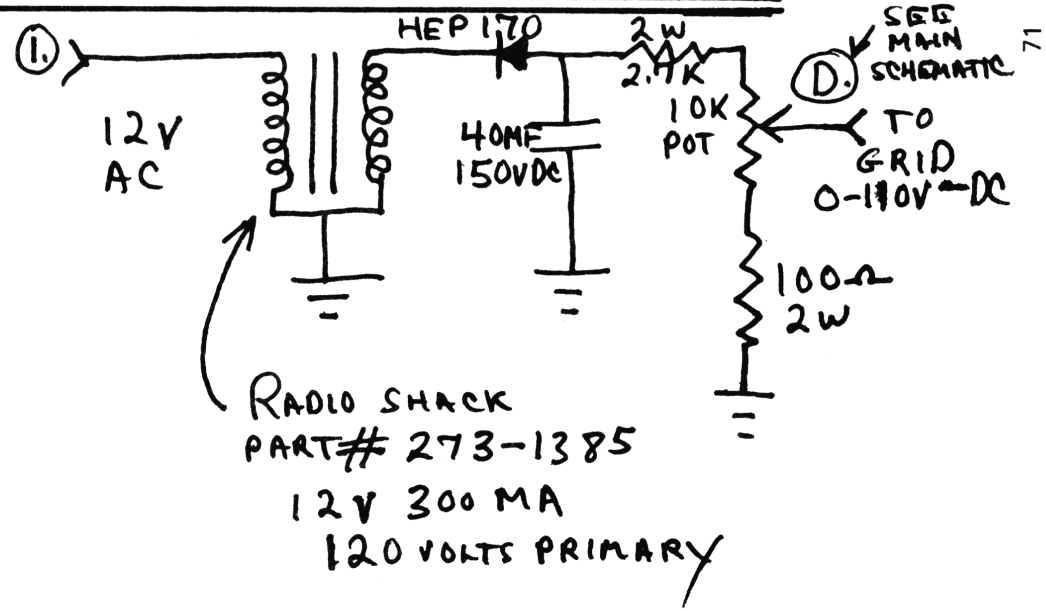

BIAS SUPPLY
SEE WHERE (1) CONNECTS TO (1) IN POWER SUPPLY